

**UNIVERSITY OF PETROLEUM AND ENERGY STUDIES**

**Assignment- II**

**Program/course:** B. Tech. (CSE)

**Subject:** Digital Electronics

**No. of pages:** 1

**Semester:** II

**Max. Marks:** 10

Q1.	Differentiate the following:  (a) Combinational and Sequential Circuits (b) Synchronous and Asynchronous Counter (c) Counter and Register (d) SIPO and PIPO Register	CO2
Q2.	Explain the following flip-flop in detail:  (a) S-R flip-flop (b) T flip-flop	CO2
Q3.	Design a 4-bit synchronous down counter that counts through all states from 1111 down to 0000.	CO2
Q4.	Design and implement J-K flip-flop using S-R flip-flop.	CO2
Q5.	Design a 4-bit Self-correcting Shift Counter using D flip-flop.	CO2
Q6.	Design a synchronous BCD counter using either J-K or D flip-flop.	CO2
Q7.	Discuss the significance of following registers of 8085 microprocessor  (a) Accumulator, i.e. register A (b) General purpose register, i.e. B, C, D, E, H, L (c) Stack Pointer (d) Program Counter (e) Instruction register (f) Temporary register (g) Status Flags	CO4
Q8.	What do you understand by timing diagram? Draw and explain the timing diagram of:  (a) Fetch operation (b) Memory write operation	CO4
Q9.	What do you understand by opcode and operand in an assembly language program. Explain the following types of instructions with the help of examples:  (a) One byte instruction (b) Two byte instruction (c) Three byte instruction	CO4
Q10.	Explain the following:  (a) Binary weighted D/A converter (b) Successive Approximation A/D converter	CO3